
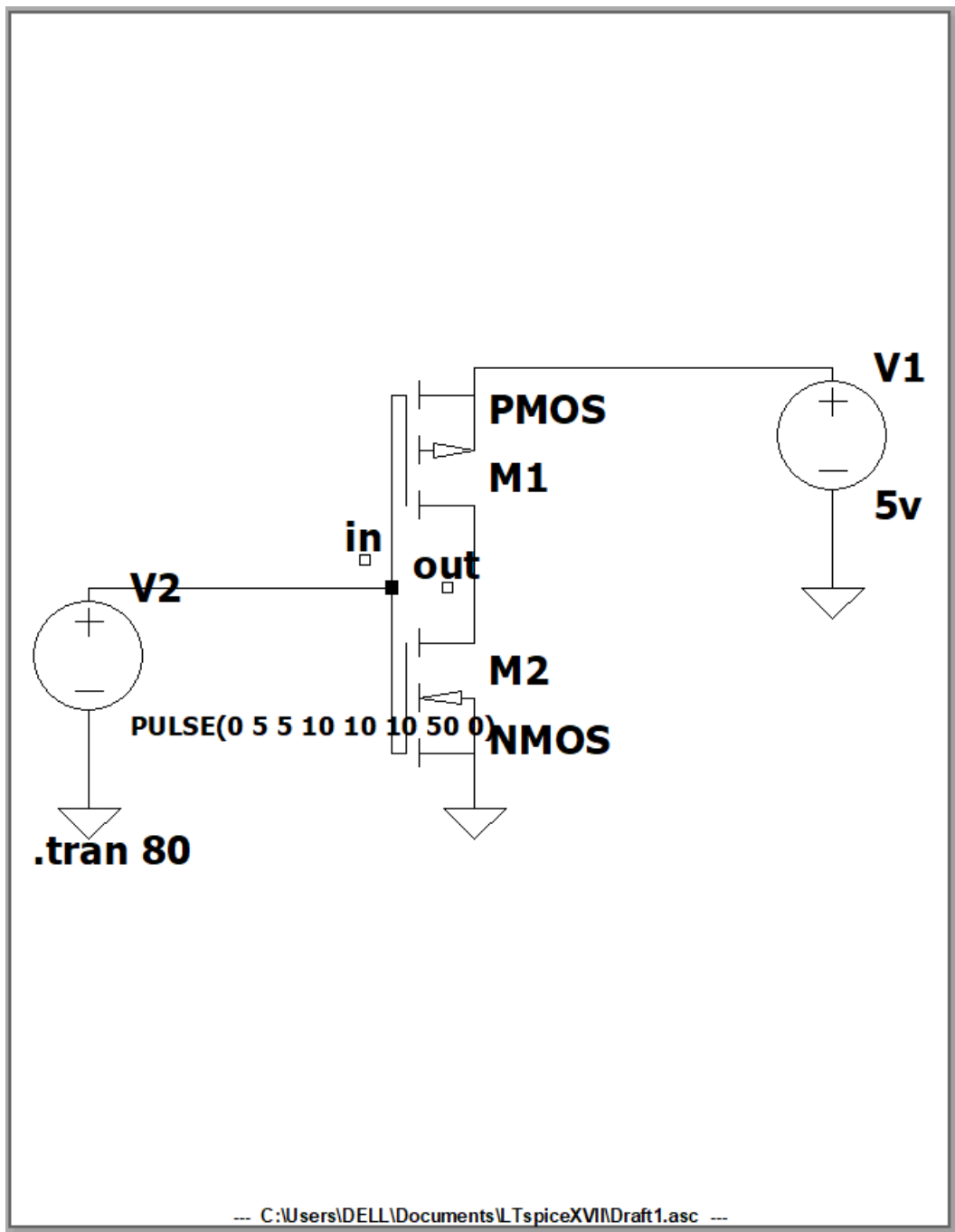



VLSI -1

 

Circuit Design of the CMOS Inverter circuit.



Graph Observation (in LTspice XVII)

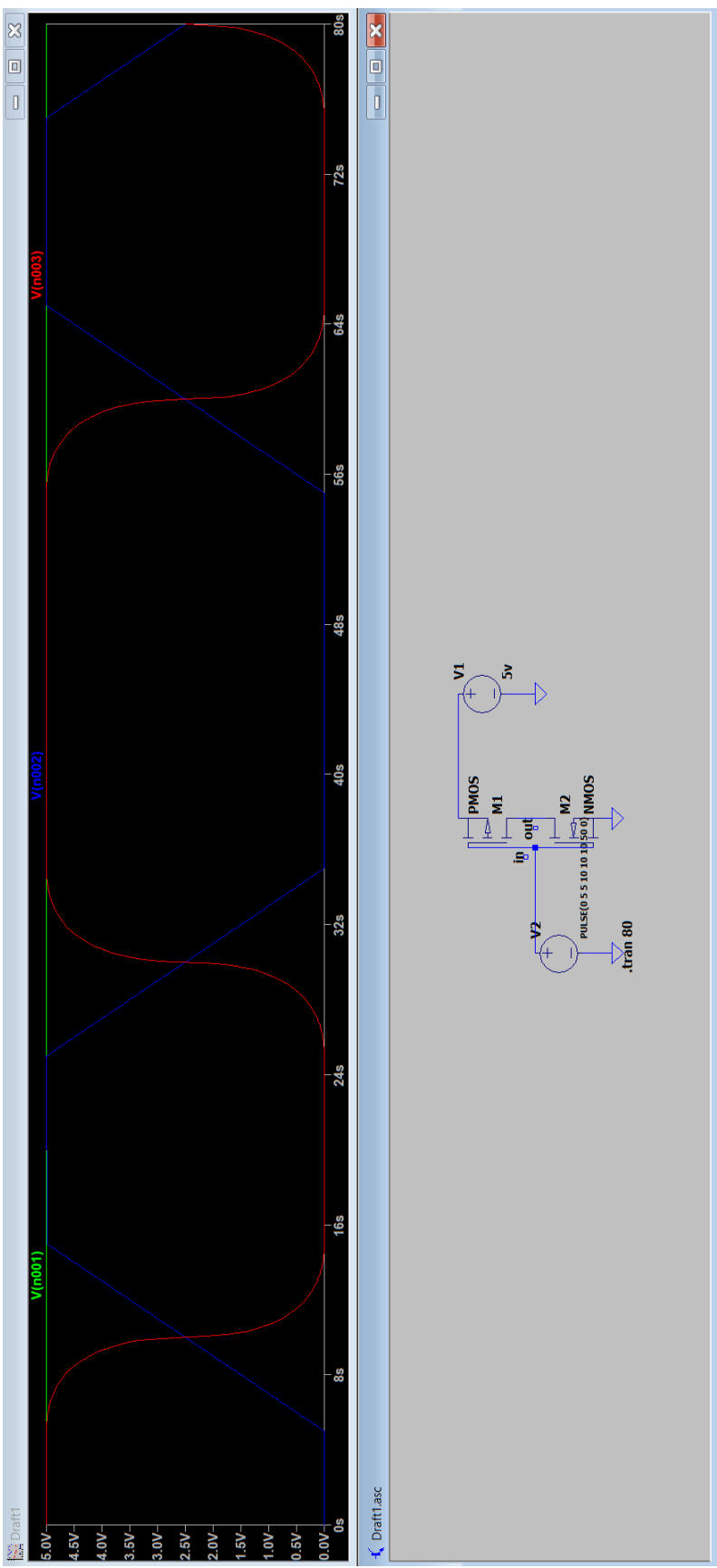

Lab Report 1: - CMOS Inverter


Name: - R. Hemanth Krishna Vineel

Roll no: - 118CS0017

Course : - VLSI Practice


VLSI -2

A. 2 input NAND gate

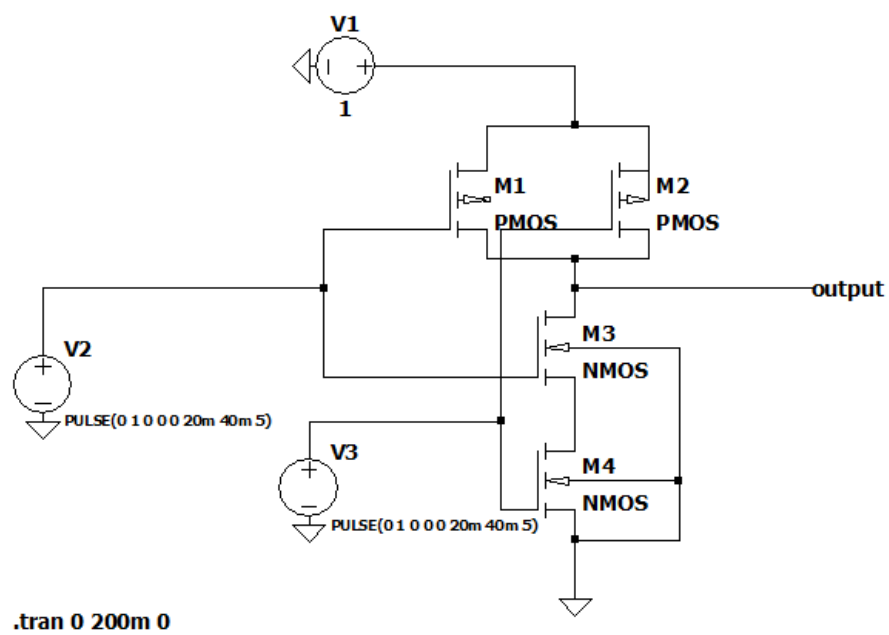


--- C:\Users\DELL\Documents\LTspiceXVII\NAND gate 2 ip.asc ---


Circuit diagram of 2 input NAND gate

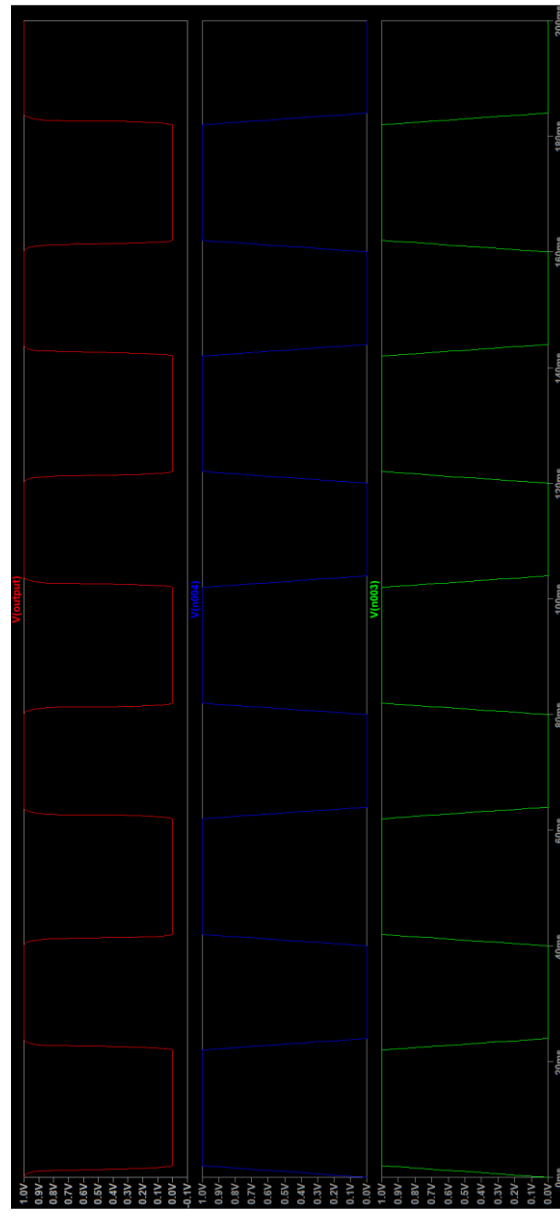


Observation graph -1

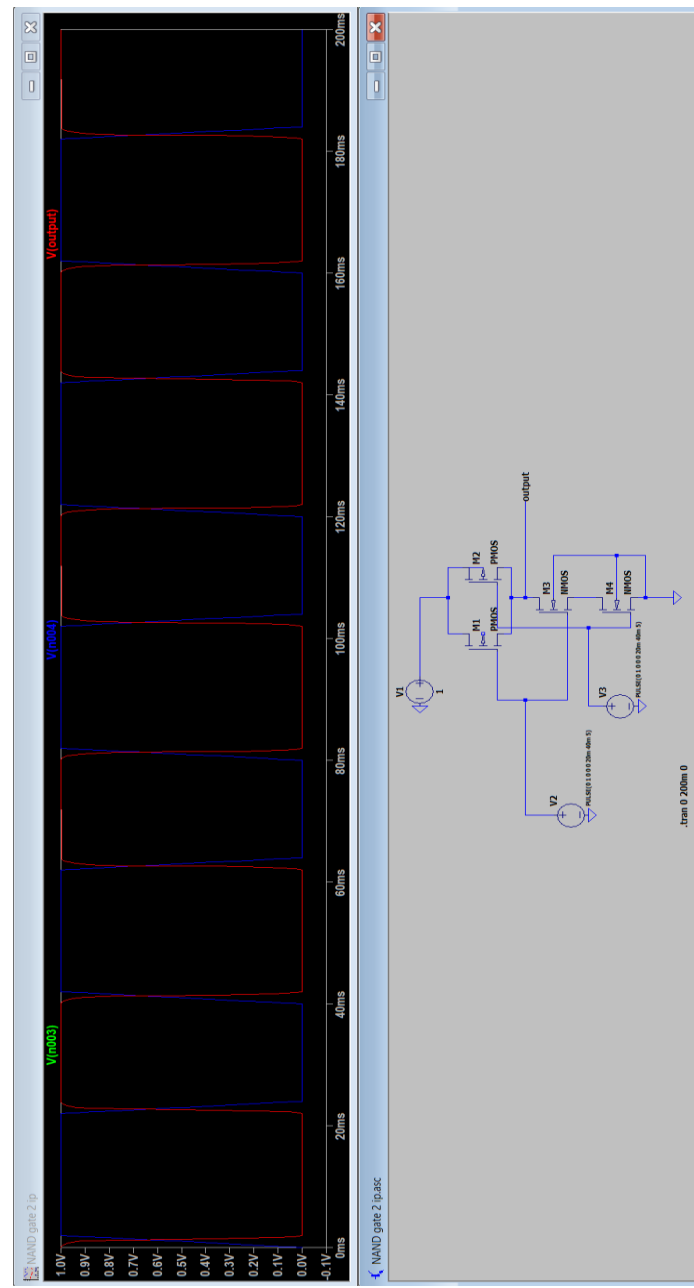

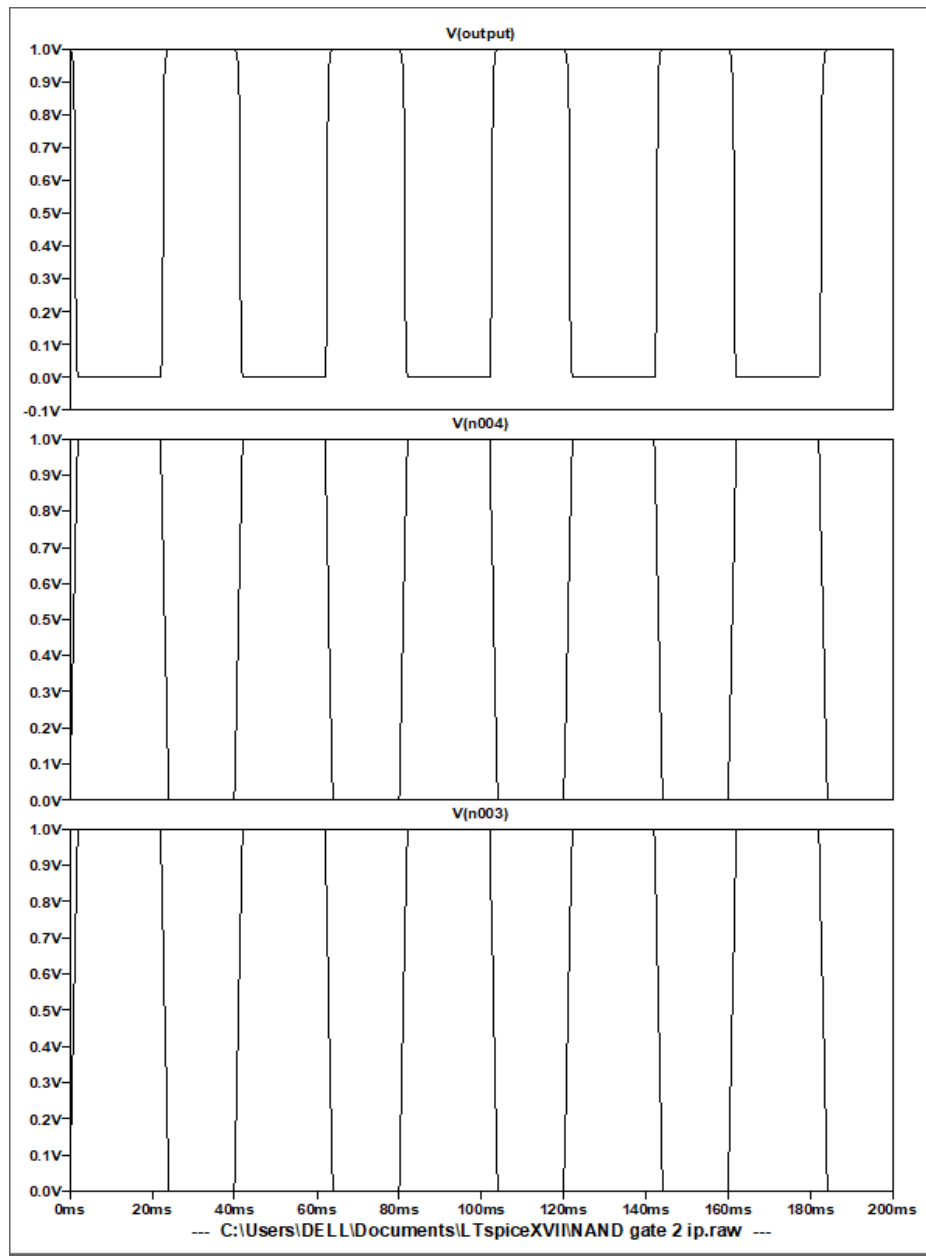Combined image of 2 input NAND gate and it's graph




Observation graph -2

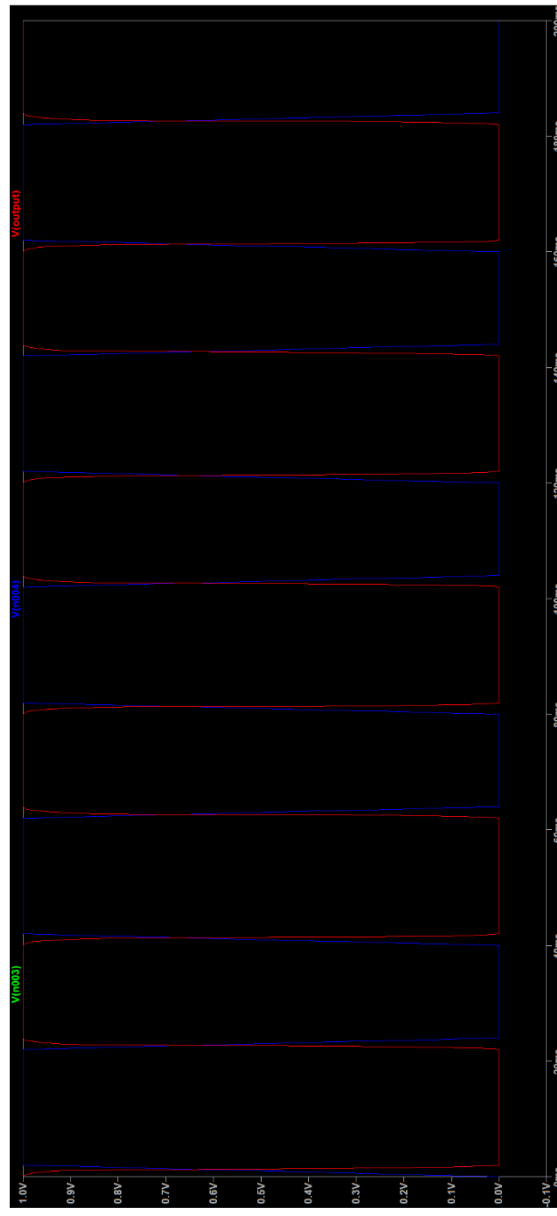


Combined graph observation

B. 2 input NOR gate

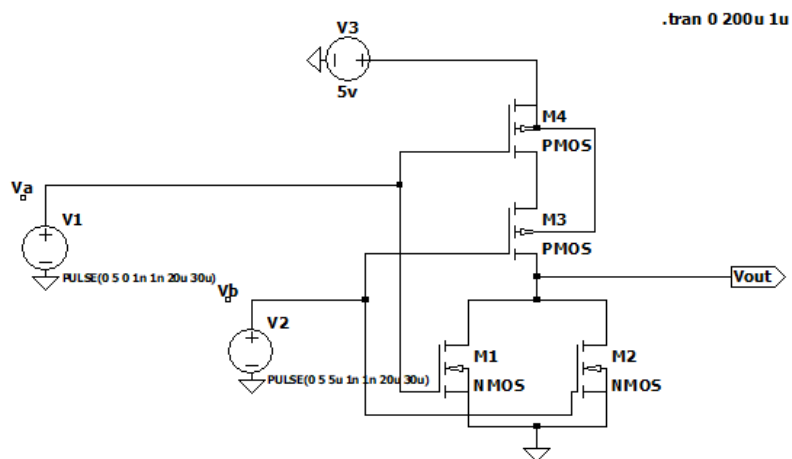


--- C:\Users\DELL\Documents\LTspiceXVII\NOR gate 2ip.asc ---

Circuit diagram of 2 input NOR gate

 


Combined graph observation

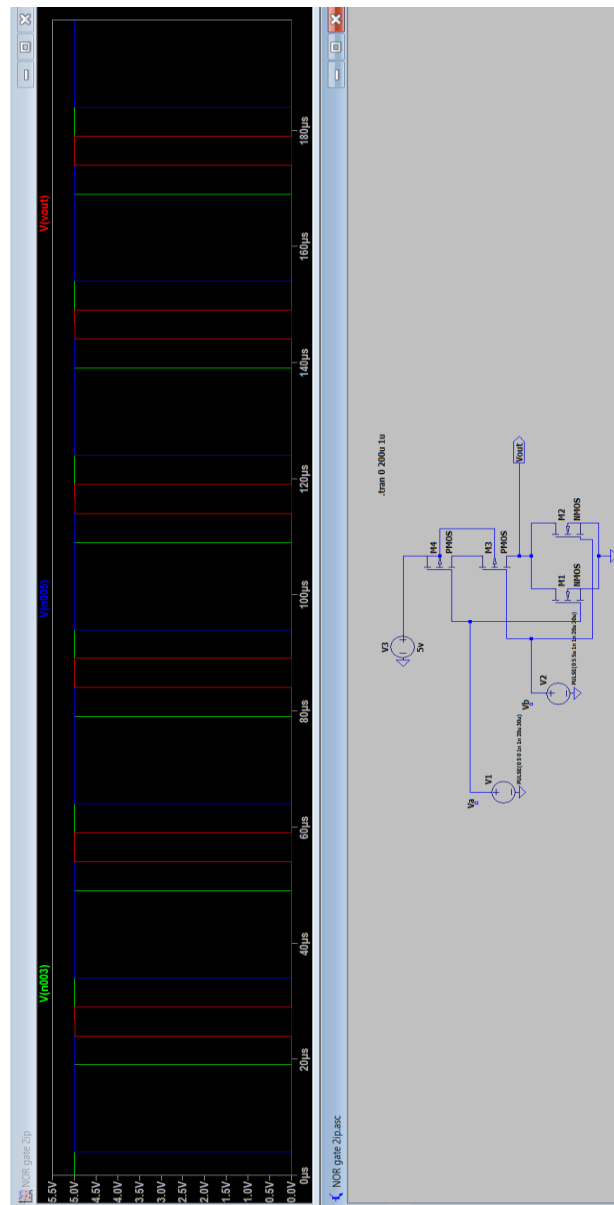

Combined image of 2 input NOR gate and it's graph



Observation Graph 1

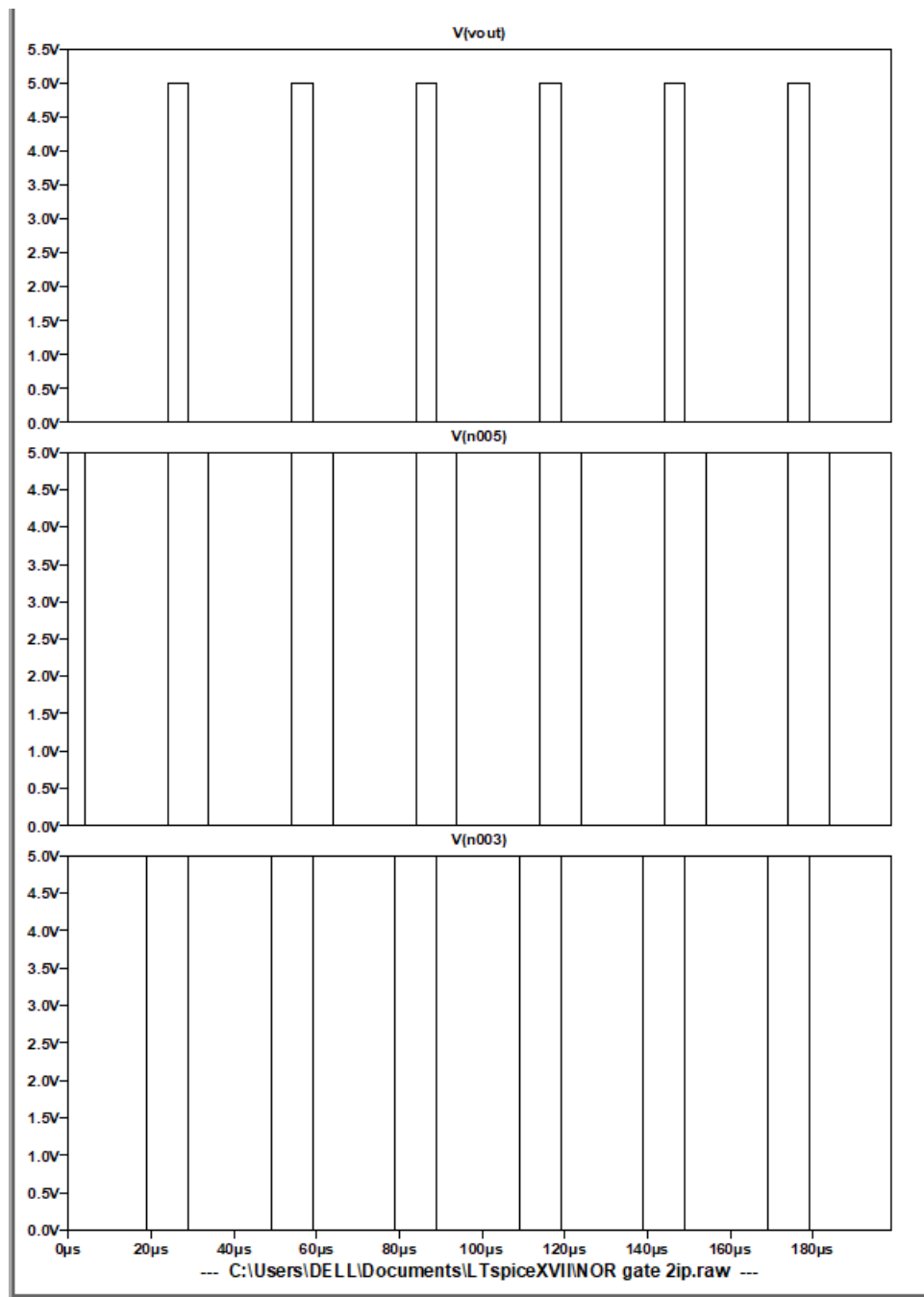

Observation graph -2

Lab Report 2: - 2 input NAND gate and 2 input NOR gate


Name: - R. Hemanth Krishna Vineel

Roll no: - 118CS0017


Course : - VLSI Practice

VLSI -3


A.3 input NAND gate

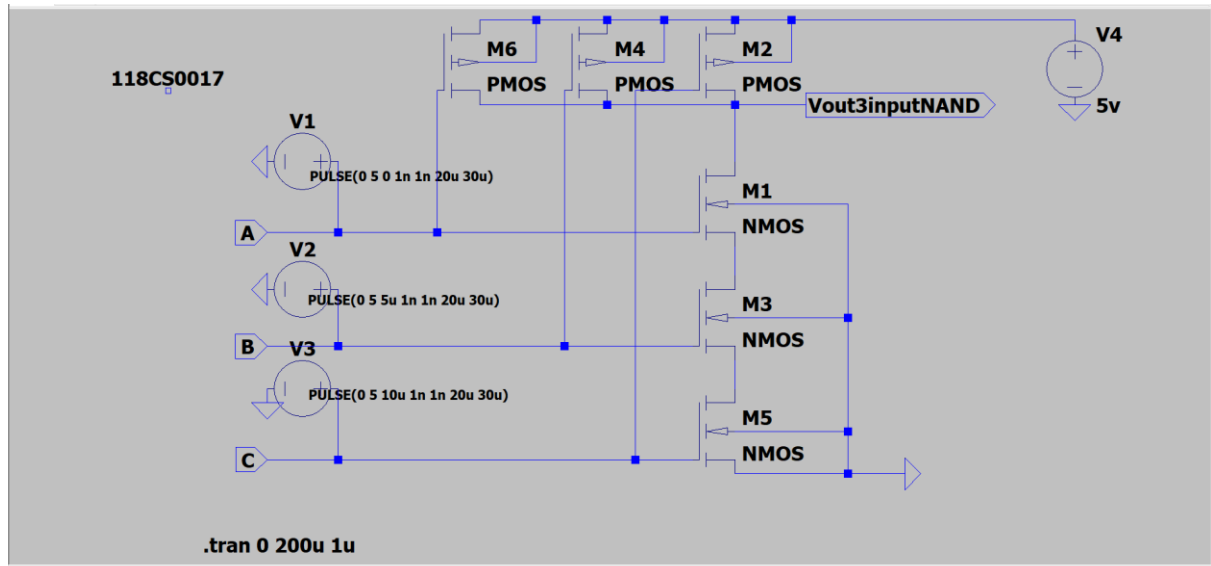

 Circuit diagram of 3 input NAND using CMOS




Observation Graph - 1

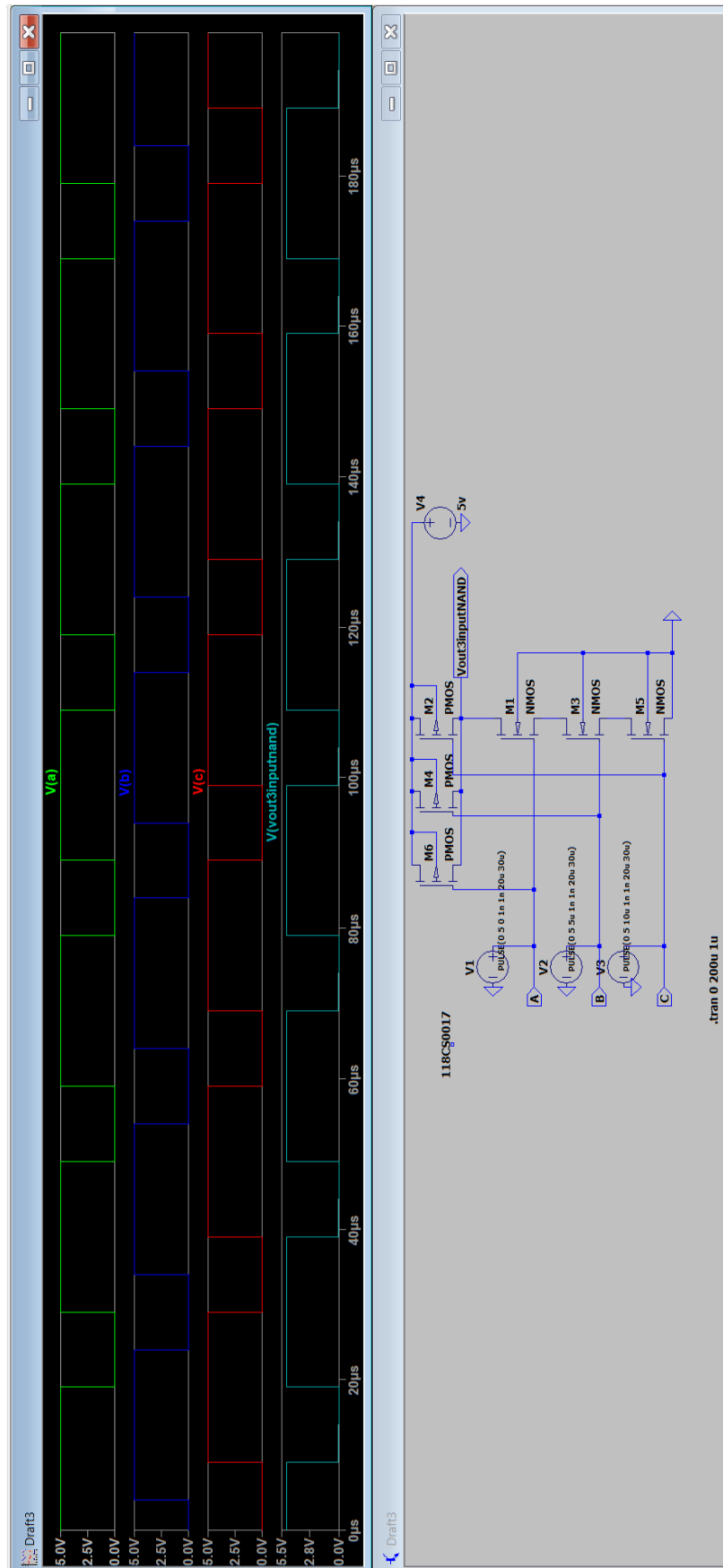


Combined picture of 3 input NAND using CMOS(Circuit and observation graph)


B.3 input NOR gate

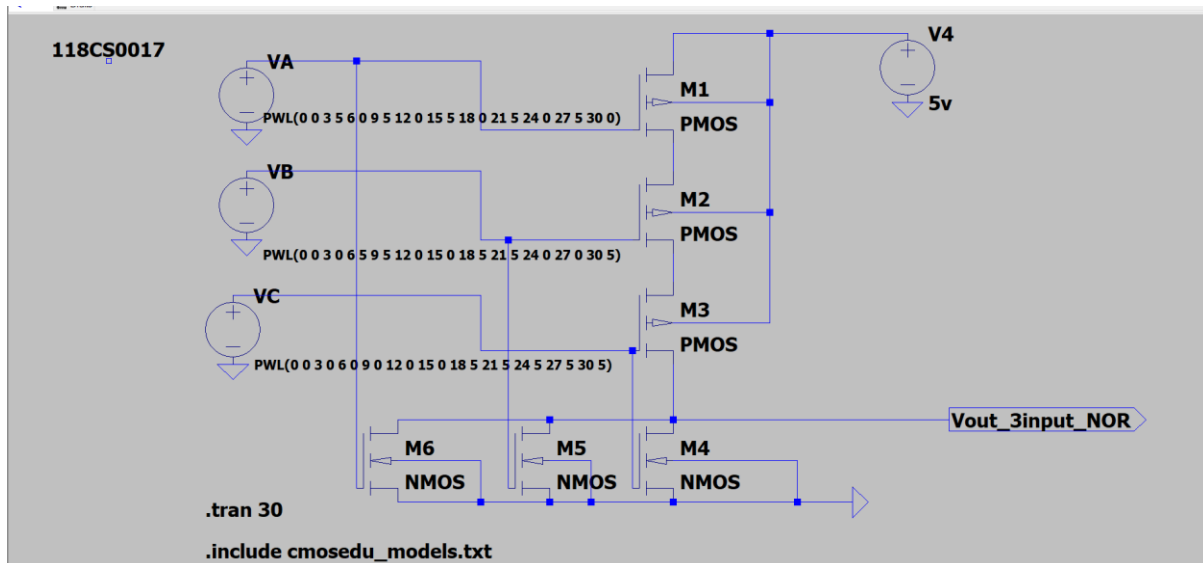

 Circuit Diagram of 3 input NOR using CMOS



Observation Graph - 2

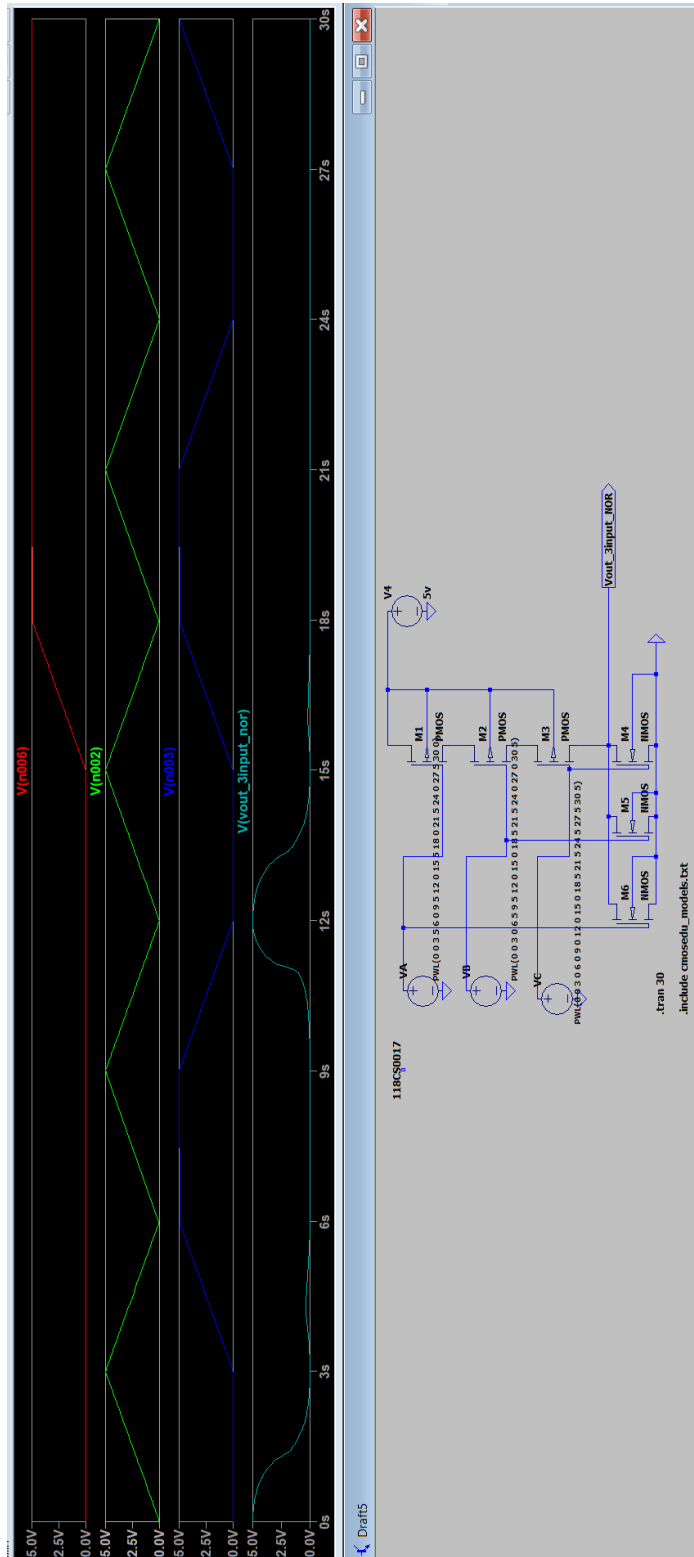

Combined picture of 3 input NOR using CMOS(Circuit and observation graph)

Lab Report 3: - 3 input NAND gate and 3 input NOR gate


Name: - R. Hemanth Krishna Vineel

Roll no: - 118CS0017


Course : - VLSI Practice

VLSI -4


A.2 Input XOR gate using CMOS

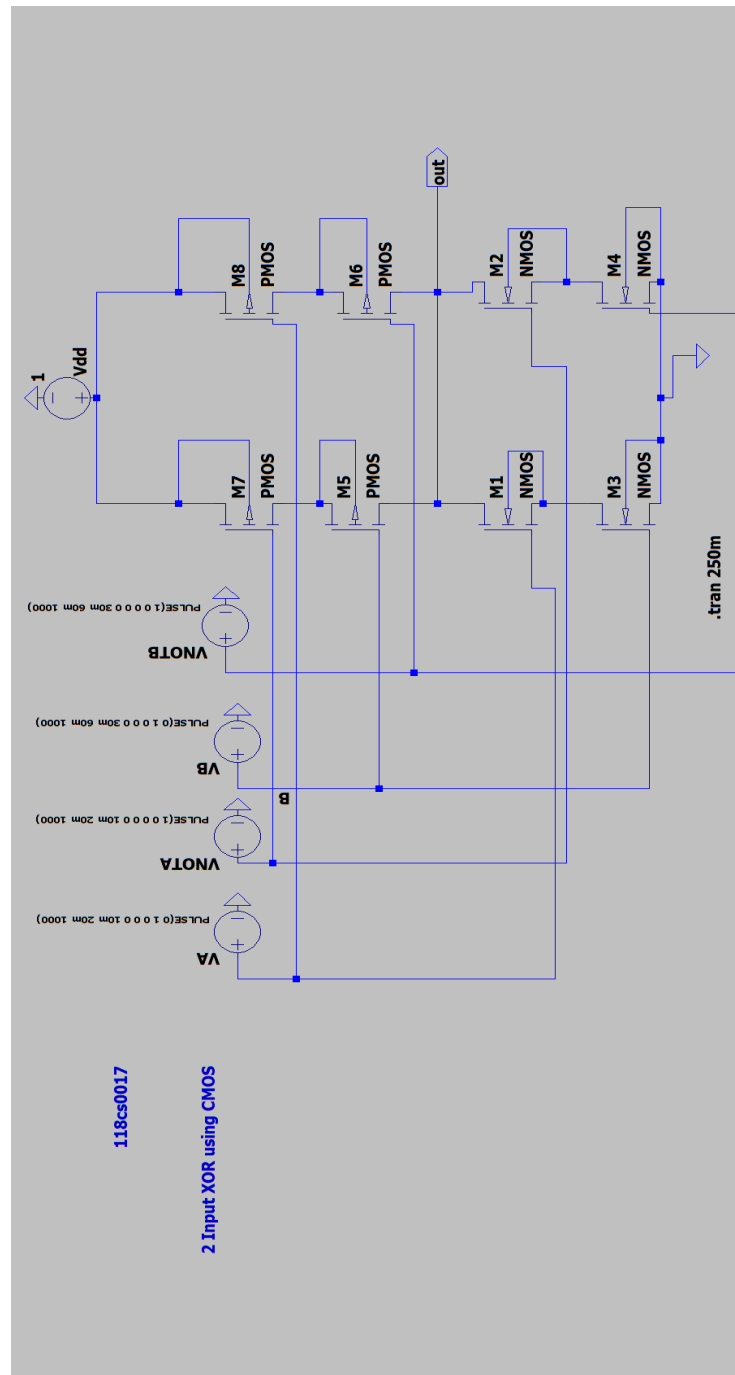

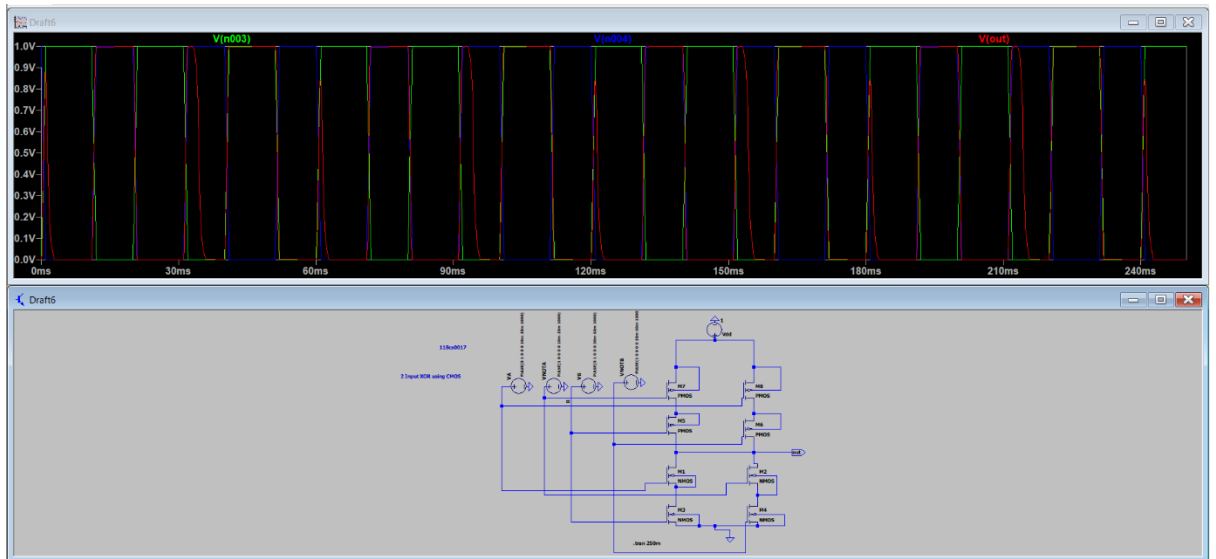Circuit Diagram of 2 input XOR using CMOS




Combined image of circuit and graph

 


Observation Graph


B.2:1 MUX using CMOS

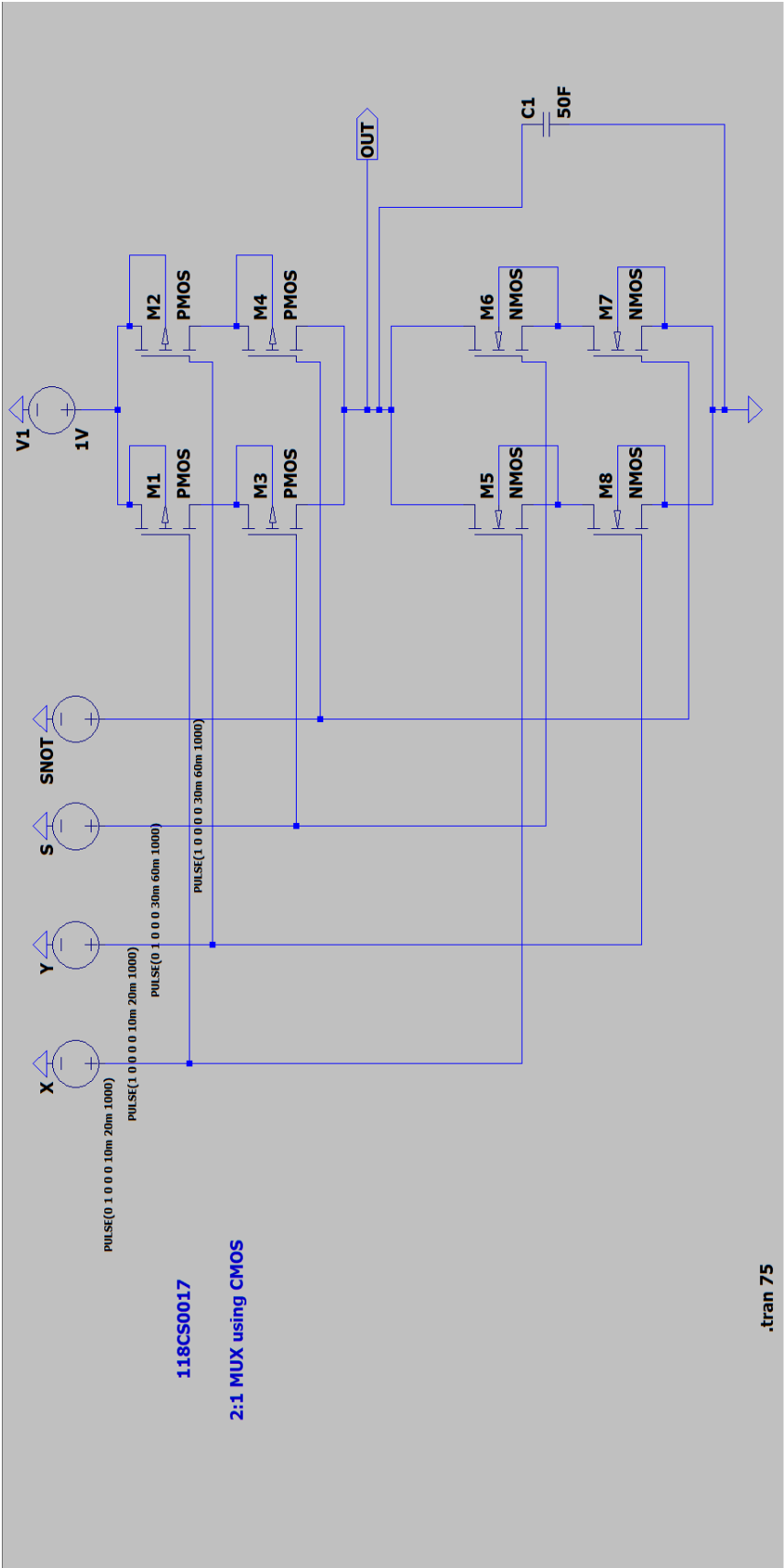

Circuit diagram of 2:1 MUX using CMOS

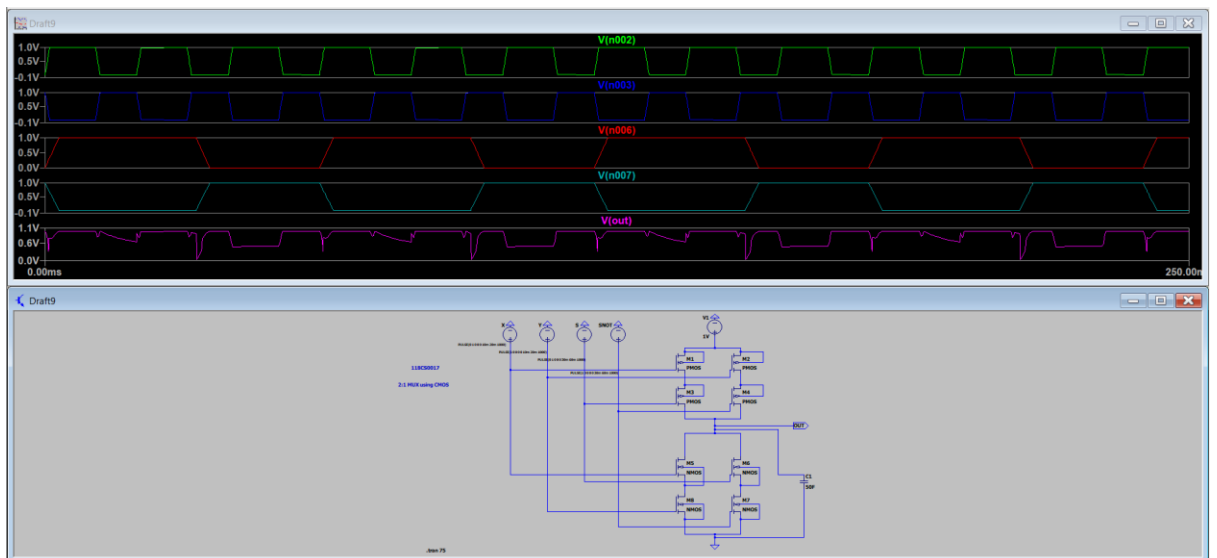


Combined image of circuit and graph

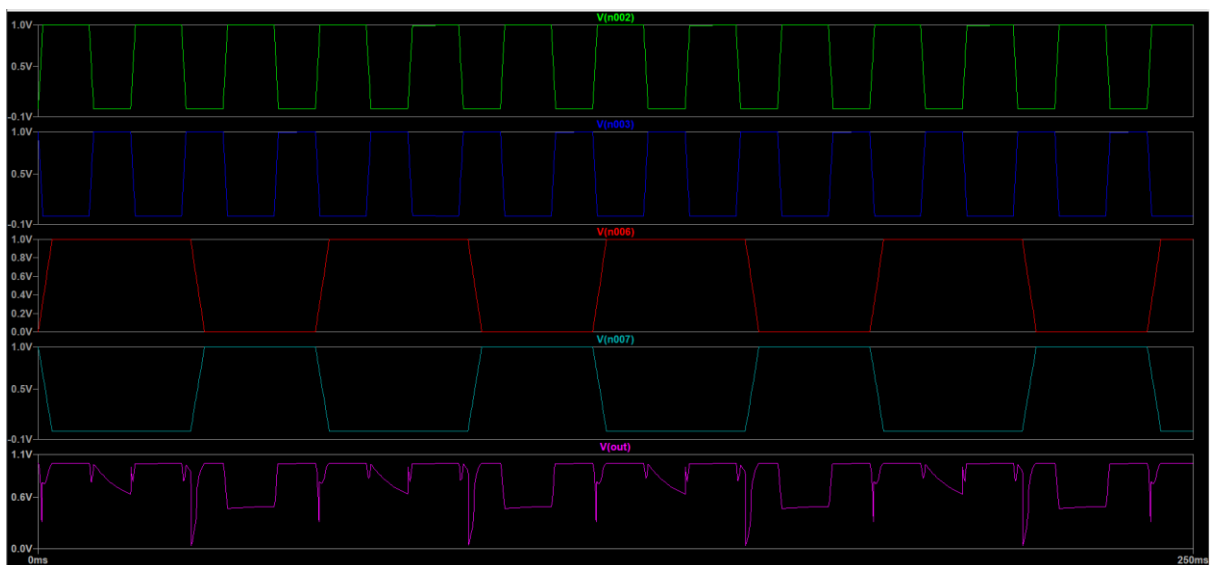


Observation Graph

VLSI LAB

a. 4:1 mux circuit design and the graph.

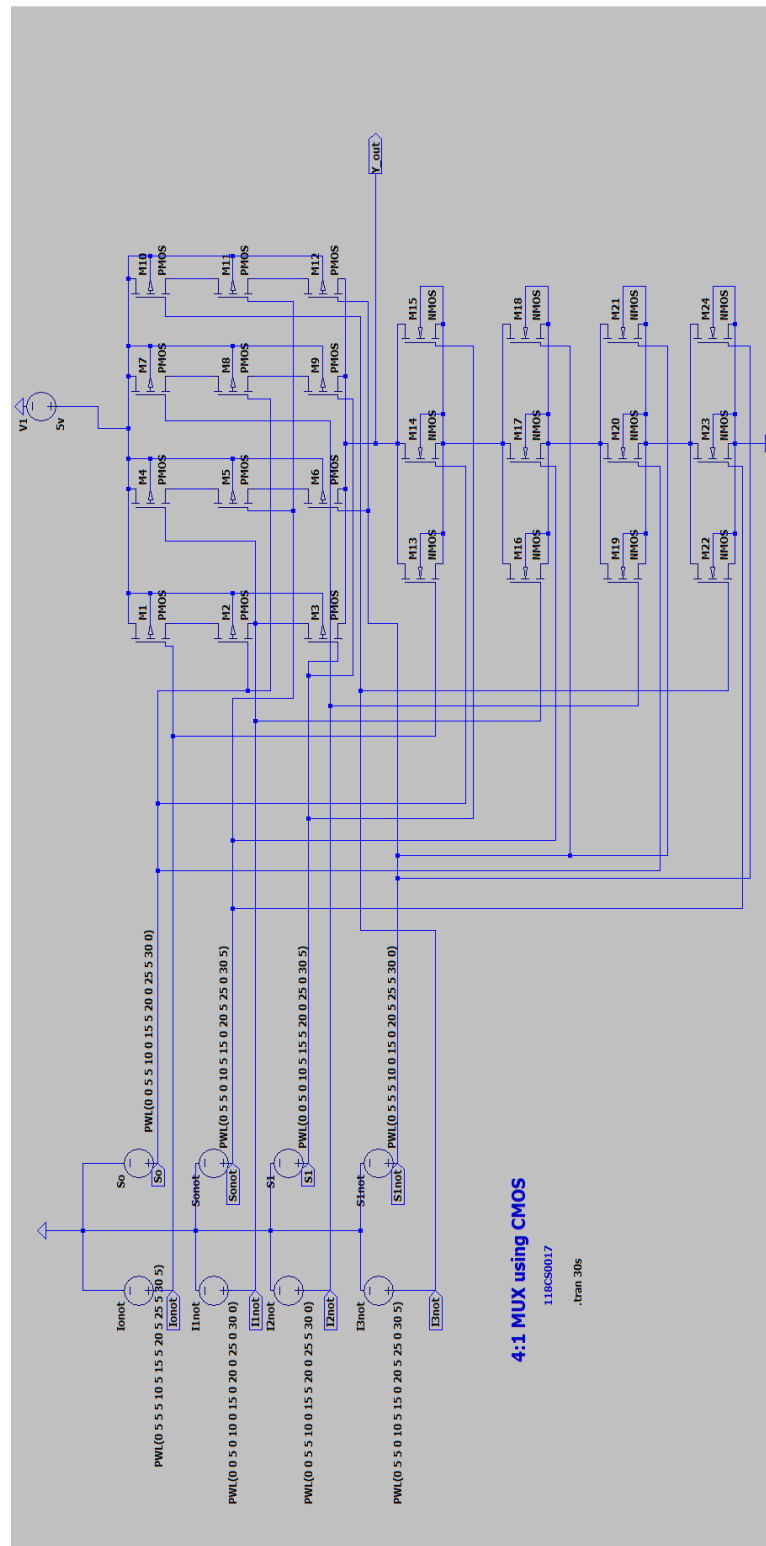

4:1 mux circuit design

 

Observation graph-1

Lab report: 4:1 MUX circuit and it's design


Name: R. Hemanth Krishna Vineel

Roll no: 118cs0017


Course: VLSI Lab practice

VLSI-5

a. 2:1 Mux using Transmission Gate.

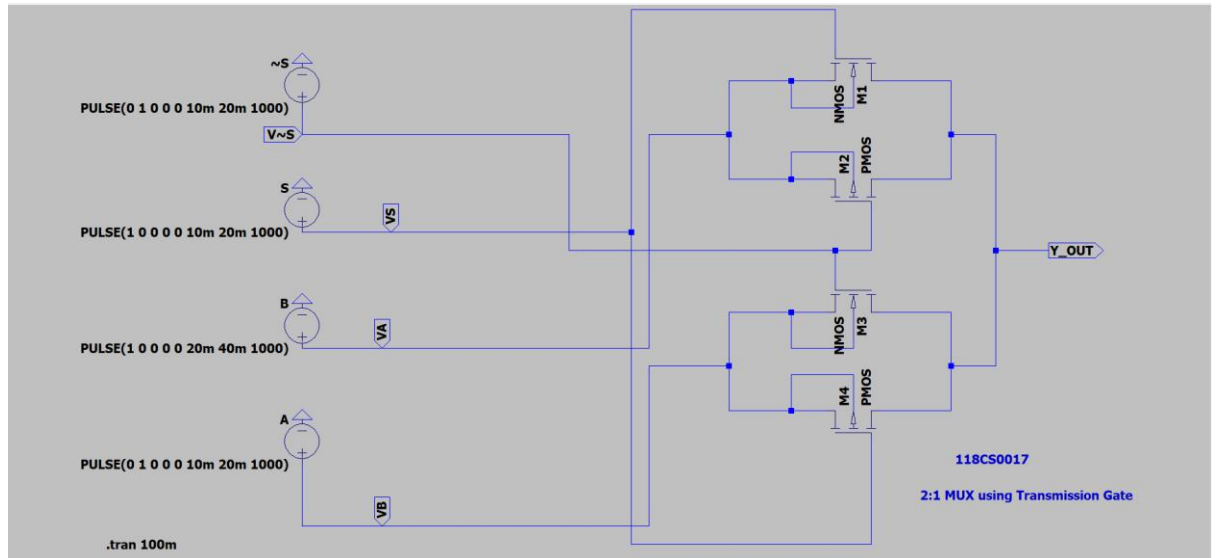


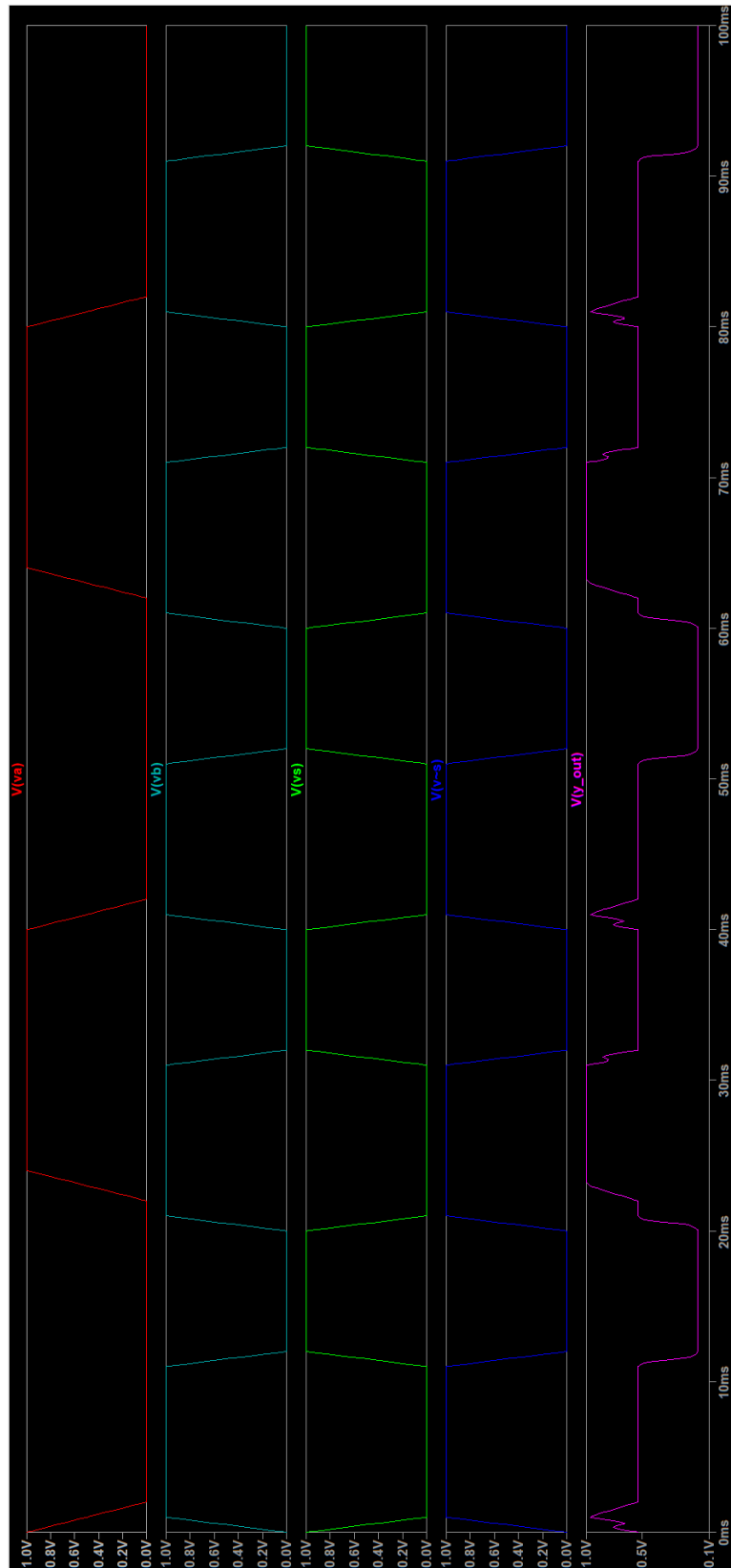Circuit diagram of 2:1 mux using Transmission Gate




Observation Graph-1

b. Tristate Inverter

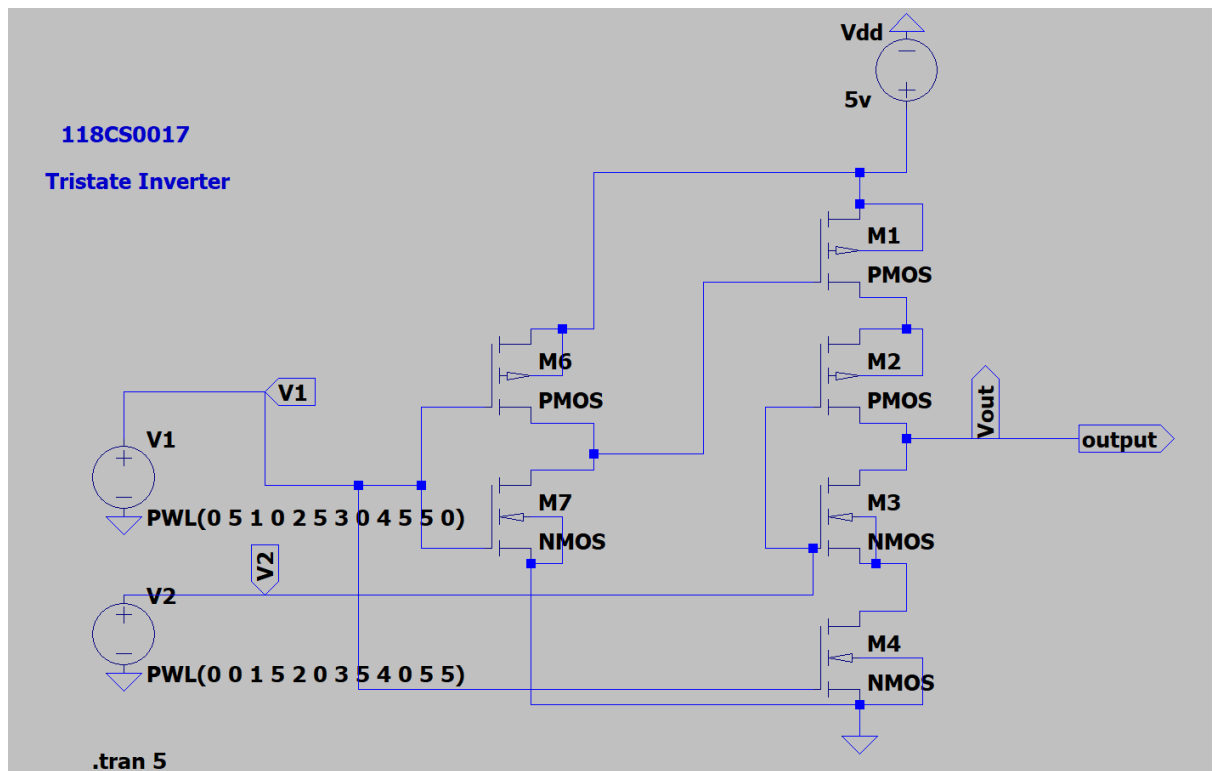

Circuit diagram of Tristate inverter

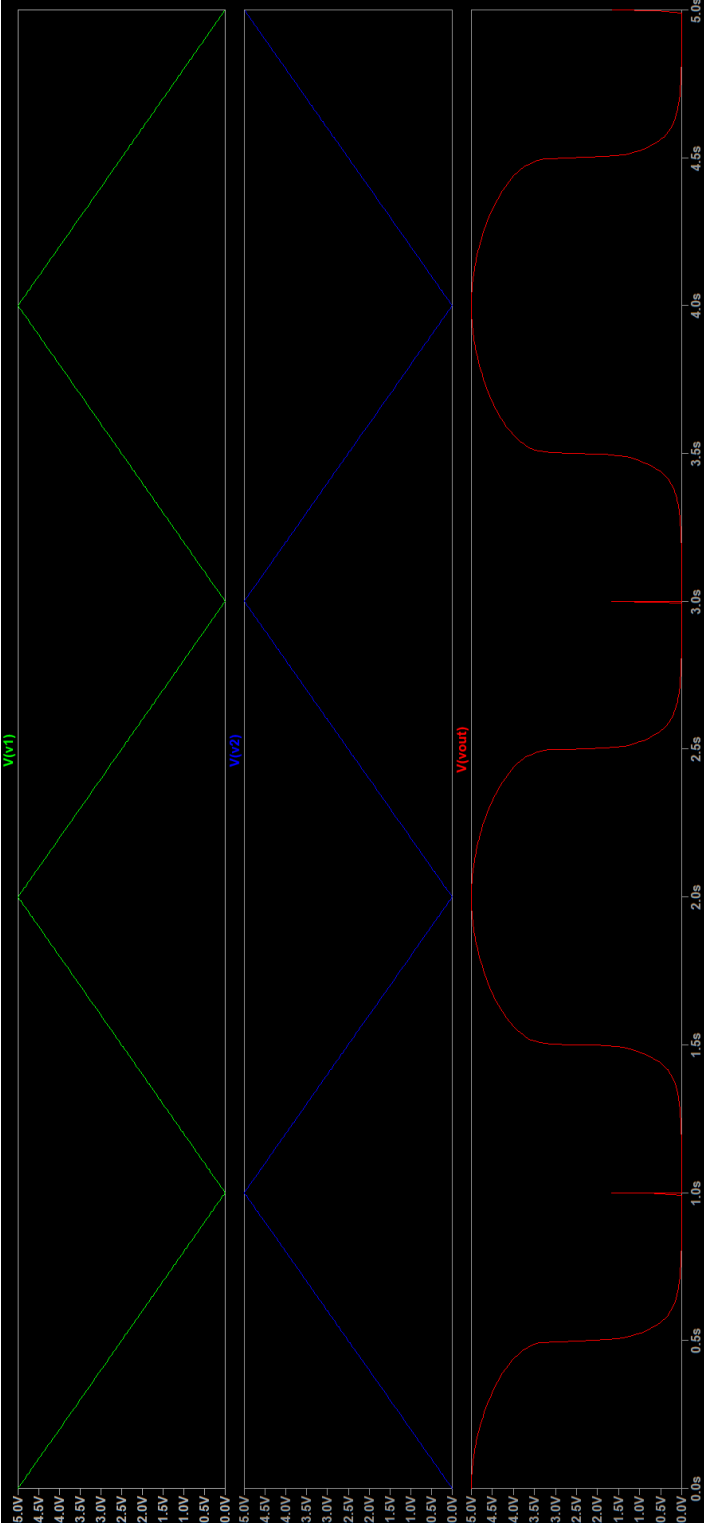

Observation Graph-2

Lab Report 5: - 2:1 mux using transmission gate and tristate inverter

Name: - R. Hemanth Krishna Vineel

Roll no: - 118CS0017

Course: - VLSI Practice